 


Homework #5

1. FSM logic chart to detect bit stream pattern "1010"



Design module

```
module det_1010 (  
    input clk, rst, in,  
    output reg flag  
);  
    // States defined using one-hot encoding  
    parameter pIdle = 5'b00001;  
    parameter p1 = 5'b00010;  
    parameter p10 = 5'b00100;  
    parameter p101 = 5'b01000;  
    parameter p1010 = 5'b10000;  
  
    reg [4:0] curSt, nxtSt;  
  
    always @(posedge clk or posedge rst) begin  
        if (rst)  
            curSt <= #1 pIdle; // Reset state to pIdle  
        else  
            curSt <= #1 nxtSt; // Update state on clock edge  
    end
```

```

always @(*) begin
    flag = 1'b0; // Default flag value
    case (curSt)
        pIdle: begin
            if (in) nxtSt = p1; // Transition to p1 on receiving '1'
            else nxtSt = pIdle; // Stay in pIdle if '0'
        end
        p1: begin
            if (in) nxtSt = p1; // Stay in p1 if '1'
            else nxtSt = p10; // Transition to p10 on receiving '0'
        end
        p10: begin
            if (in) nxtSt = p101; // Transition to p101 on receiving '1'
            else nxtSt = pIdle; // Return to pIdle if '0'
        end
        p101: begin
            if (in) nxtSt = p1010; // Transition to p1010 on receiving '1'
            else nxtSt = pIdle; // Return to pIdle if '0'
        end
        p1010: begin
            flag = 1'b1; // Set flag when `1010` is detected
            nxtSt = pIdle; // Return to pIdle state
        end
        default: nxtSt = pIdle; // Default state is pIdle
    endcase
end
endmodule

```

Testbench Module

```

module tb_det_1010();
    reg clk, rst, in;
    wire flag;

    // Instantiate the FSM module
    det_1010 u0 (.clk(clk), .rst(rst), .in(in), .flag(flag));

    initial begin
        // Initialize signals
    end
endmodule

```

```

    clk = 0;
    rst = 0;
    in = 0;

    // Apply reset
    #2 rst = 1;
    #3 rst = 0;


    // Apply test pattern `1010`
    #5 in = 1;
    #5 in = 0;
    #5 in = 1;
    #5 in = 0;
    #5 $finish; // End simulation
end

// Generate clock signal
always #3 clk = ~clk;

// Monitor output
initial begin
    $monitor("At time %t, flag = %b, input = %b", $time, flag, in);
end
endmodule

```

Output

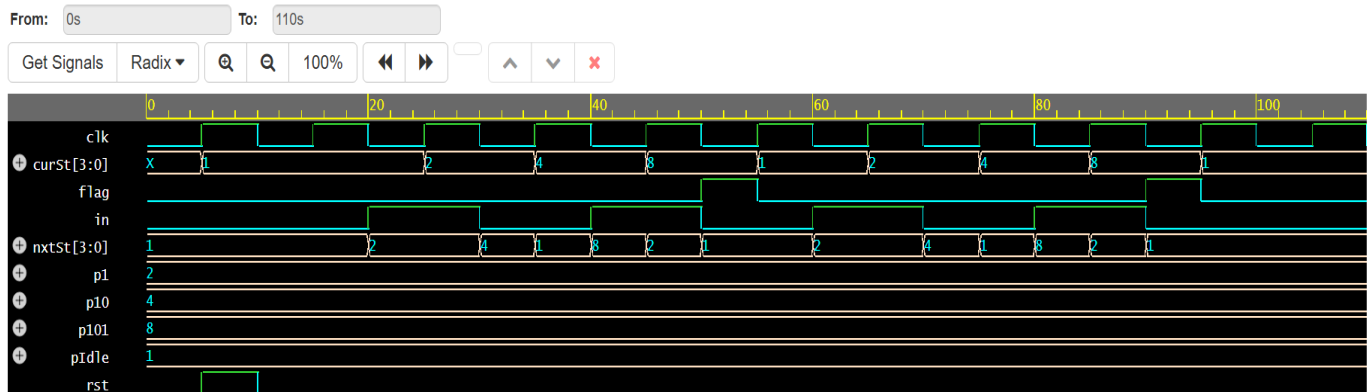


```

[2024-11-27 10:12:39 UTC] iverilog '-Wall' '-g2012' design.sv testbench.sv &&
unbuffer vvp a.out
At time          0, flag = 0, input = 0
At time         10, flag = 0, input = 1
At time         15, flag = 0, input = 0

```

At time 20, flag = 0, input = 1
 At time 25, flag = 0, input = 0
 testbench.sv:23: \$finish called at 30 (1s)
 Done

 2. FSM to detect bit streams which could be divided by 7



Design Module

```

module div_7(
    input clk,
    input rst,
    input in,
    output reg flag
);

```

```

// Define states for remainders 0 to 6 (one-hot encoding)

```

```

parameter pRem_0 = 7'b00000001;

```

```

parameter pRem_1 = 7'b00000010;

```

```

parameter pRem_2 = 7'b00000100;

```

```

parameter pRem_3 = 7'b00001000;

```

```

parameter pRem_4 = 7'b00010000;

```

```

parameter pRem_5 = 7'b00100000;

```

```

parameter pRem_6 = 7'b01000000;

```

```

reg [6:0] curSt, nxtSt;

```

```

always @(posedge clk) begin
    if (rst) curSt <= pRem_0; // Start at remainder 0 on reset
    else curSt <= nxtSt;
end

always @(*) begin
    flag = 0; // Default flag value
    case(curSt)
        pRem_0: begin
            if (in) nxtSt = pRem_1; // Shift to remainder 1 if input is 1
            else nxtSt = pRem_0; // Stay in remainder 0 if input is 0
        end
        pRem_1: begin
            if (in) nxtSt = pRem_2;
            else nxtSt = pRem_3;
        end
        pRem_2: begin
            if (in) nxtSt = pRem_4;
            else nxtSt = pRem_5;
        end
        pRem_3: begin
            if (in) nxtSt = pRem_6;
            else nxtSt = pRem_0;
        end
        pRem_4: begin
            if (in) nxtSt = pRem_1;
            else nxtSt = pRem_2;
        end
        pRem_5: begin
            if (in) nxtSt = pRem_3;
            else nxtSt = pRem_4;
        end
        pRem_6: begin
            if (in) nxtSt = pRem_5;
            else nxtSt = pRem_6;
            flag = 1; // Divisible by 7 when remainder is 0 after 7th bit
        end
        default: nxtSt = pRem_0; // Default state is remainder 0
    endcase
end

```

```
end  
endmodule
```

Testbench Module

```
module tb_div_7_tb;
```

```
    reg clk, rst, in;  
    wire flag;
```

```
    // Instantiate the div_7 module
```

```
    div_7 uut (
```

```
        .clk(clk),
```

```
        .rst(rst),
```

```
        .in(in),
```

```
        .flag(flag)
```

```
    );
```

```
    // Clock generation
```

```
    always #5 clk = ~clk; // Clock period of 10 time units
```

```
    // Initial block to initialize signals and apply test vectors
```

```
    initial begin
```

```
        clk = 0;
```

```
        rst = 0;
```

```
        in = 0;
```

```
        // Apply reset
```

```
        #10 rst = 1;
```

```
        #10 rst = 0;
```

```
        // Test input sequence for 7 (divisible by 7)
```

```
        #10 in = 1;
```

```
        #10 in = 0;
```

```
        #10 in = 0;
```

```
        #10 in = 0;
```

```
        #10 in = 1;
```

```
        #10 in = 0;
```

```
        #10 in = 0; // Divisible by 7, flag should be high
```

```
        #20; // Wait a bit for simulation to reflect output
```



```

    input reset,
    input [7:0] duty_cycle, // 0-100% duty cycle
    output reg pwm_signal
);

    reg [7:0] counter; // Counter for PWM signal generation
    reg [7:0] duty_limit;

    always @(posedge clk or posedge reset) begin
        if (reset) begin
            counter <= 8'd0;
            pwm_signal <= 0;
            duty_limit <= 8'd0;
        end else begin
            duty_limit <= duty_cycle; // Set duty cycle limit
            if (counter < 8'd100) begin
                counter <= counter + 8'd1;
            end else begin
                counter <= 8'd0;
            end
        end

        // PWM signal logic
        if (counter < duty_limit)
            pwm_signal <= 1;
        else
            pwm_signal <= 0;
        end
    end

endmodule

```

Testbench module

```

module testbench;
    reg clk;
    reg reset;
    reg [7:0] duty_cycle;
    wire pwm_signal;

    // Instantiate the DUT (Design Under Test)
    duty_cycle_calculator dut (

```



```

        .clk(clk),
        .reset(reset),
        .duty_cycle(duty_cycle),
        .pwm_signal(pwm_signal)
    );

    // Clock generation
    always begin
        #5 clk = ~clk; // Clock period = 10 time units
    end

    initial begin
        // Initialize signals
        clk = 0;
        reset = 1;
        duty_cycle = 8'd50; // Start with 50% duty cycle

        // Dump waveform data to VCD file
        $dumpfile("waveform.vcd");
        $dumpvars(0, testbench);

        // Reset DUT
        #10 reset = 0;

        // Test different duty cycles
        #10 duty_cycle = 8'd10; // 10% duty cycle
        #100 duty_cycle = 8'd50; // 50% duty cycle
        #100 duty_cycle = 8'd90; // 90% duty cycle
        #100 duty_cycle = 8'd100; // 100% duty cycle

        // Finish simulation
        #500 $finish;
    end

    // Monitor the output for debugging
    initial begin
        $monitor("Time: %t | PWM Signal: %b | Duty Cycle: %0d%%", $time, pwm_signal, duty_cycle);
    end
endmodule

```

Output

```
[2024-11-27 22:03:11 UTC] iverilog '-Wall' '-g2012' design.sv testbench.sv &&  
unbuffer vvp a.out
```

VCD info: dumpfile waveform.vcd opened for output.
Time: 0 | PWM Signal: 0 | Duty Cycle: 50%
Time: 20 | PWM Signal: 0 | Duty Cycle: 10%
Time: 25 | PWM Signal: 1 | Duty Cycle: 10%
Time: 115 | PWM Signal: 0 | Duty Cycle: 10%
Time: 120 | PWM Signal: 0 | Duty Cycle: 50%
Time: 135 | PWM Signal: 1 | Duty Cycle: 50%
Time: 220 | PWM Signal: 1 | Duty Cycle: 90%
Time: 320 | PWM Signal: 1 | Duty Cycle: 100%
testbench.sv:40: \$finish called at 820 (1s)
Done

